



## Investigation of the dependence of the current on the voltage in the circuit section. Checking Ohm's Law.

### Purpose of work:

Establish experimentally the dependence of the current strength on voltage and resistance.

---

### Equipment:

040 - Am laboratory meter,  
041 - laboratory voltmeter,  
043 - power supply,  
073 - 1 Ohm resistor,  
074 - 2 Ohm resistor,  
075 - 4 Ohm resistor,  
045 - rheostat,  
042 - Current circuit key,

---


### Theory:

In this work must be convinced of the validity of Ohm's law for a section of the circuit.

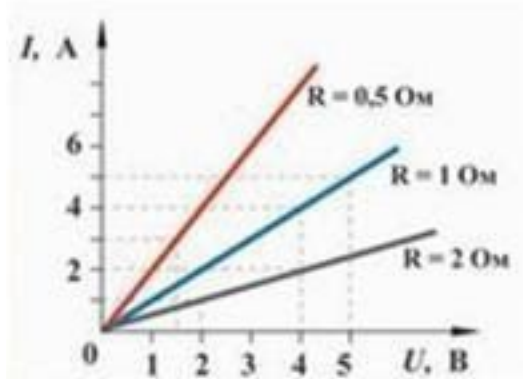**Ohm's law for a homogeneous section of a chain: *the current in a conductor is directly proportional to the applied voltage and inversely proportional to the resistance of the conductor.***

$$I = \frac{U}{R}$$


Graphical dependence of the current I on the voltage U - volt-ampere characteristic



---

**On the board:**

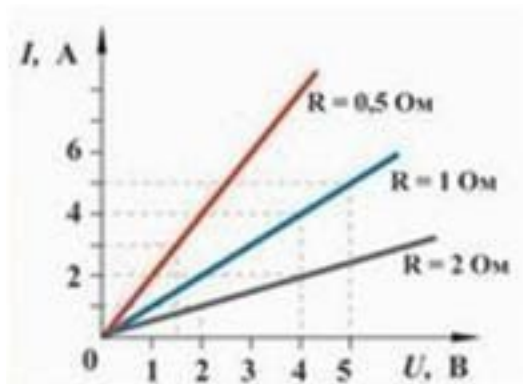
**Ohm's law for a homogeneous section of the circuit: *the current in a conductor is directly proportional to the applied voltage and inversely proportional to the resistance of the conductor.***



---

**Work progress:**

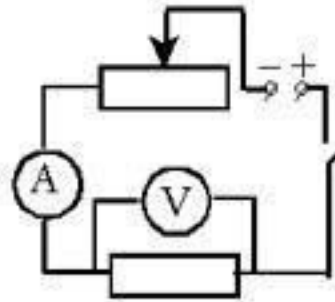1. Assemble the electrical circuit No. 1 shown in the figure. voltage value voltage at the Set the source to 8 V. Start the simulation.



2. Change the resistance of the rheostat. Enter the results obtained on the measuring devices into table No. 1.

3. Repeat the experiment several times.

4. Table # 1.

n	Voltage, U, V	Current, I, A
1		
2		
3		

5. Carry out three measurements of the electrical circuit parameters, while adding resistors with a resistance of 1 Ohm, 2 Ohm, 4 Ohm to the electrical circuit No. 1. Using a rheostat, control the voltage across the circuit at 1 V. For each measurement, enter the resistance (R) and current (I) values in Table 2.

6. Table No. 2.

	Section resistance, R, Ohm	Current strength, I, A
1		
2		
3		

7. Make a conclusion.

**A.** We made sure that the current in the section of the circuit is directly proportional to the voltage in this section and inversely proportional to its resistance.

**In.** We made sure that the current in the section of the circuit is inversely proportional to the voltage in this section and is directly proportional to its resistance.

**C.** Make sure that the current in the section of the circuit is equal to the product of voltage and resistance.